

EEE 120: Extra Credit Design Problem

Design a synchronous counter that counts up 0, 1, 2, 3, 0, 1, 2, 3, ... when an input $x = 1$, and down when $x = 0$ using

- (a) D flip-flops.
- (b) J-K flip-flops.

You need to show the state definition table, the state transition diagram, the state transition table, the K-maps for the respective logic functions and the schematic of the implementation using flip-flops and logic gates in (a) as well as the K-maps for the logic functions and the schematic in (b).
(5 points each, 35 points total)


Note:

- 1) You can either create an electronic document and submit your answer in a **word** or **pdf** format.
- 2) Or you can work on a scratch paper and scan your answer with a scanner. If you don't have a scanner you may use a camera such as on a computer or a phone to take a picture. Transfer your picture to your computer and upload your picture in **.pdf** or **.jpg** format.
- 3) You are welcome to simulate your design using Logisim to verify its functionality but it is NOT required.

State Definition Table

State	Definition	Binary
S0	Reset, 0	00
S1	1	01
S2	2	11
S3	3	10

State Transition Diagram

 

State Transition Table

X	D _a	D _b	D _a + D _b +	
0	0	0	1	1
0	0	1	0	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

K-Maps

		D _a D _b			
		00	01	11	10
X	0	1	0	1	0
	1	0	1	0	1

		D _a D _b			
		00	01	11	10
X	0	1	0	0	1
	1	1	0	0	1

$$\bar{X} \bar{D}_a \bar{D}_b + X \bar{D}_a \bar{D}_b + \bar{X} D_a D_b + X D_a D_b$$

$$\bar{X} D_a D_b + \bar{X} D_a \bar{D}_b + X \bar{D}_a D_b + X D_a \bar{D}_b$$

$$\bar{X} (D_a + D_b)' + X (D_a + D_b)$$

$$X (D_a + D_b)$$

$$D_b = \bar{D}_b$$

